

## Cpr E 281 LAB2

ELECTRICAL AND COMPUTER  
ENGINEERING  
IOWA STATE UNIVERSITY

## Lab 2 Answer Sheet

Name and Student ID: Hosam AbdelHawab, 838973177 Lab Section: KDate: Sept 6, 2016


## PRELAB:

- Q1. Read section 3.0 and fill in the truth table below for *lab2step1*. Then use it to construct the SOP expression and draw the resulting circuit using logic gates.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

SOP Logic Expression:  $(\bar{A}\bar{B}\bar{C}) + (A\bar{B}\bar{C}) + (AB\bar{C}) = F$ 

Circuit Diagram:

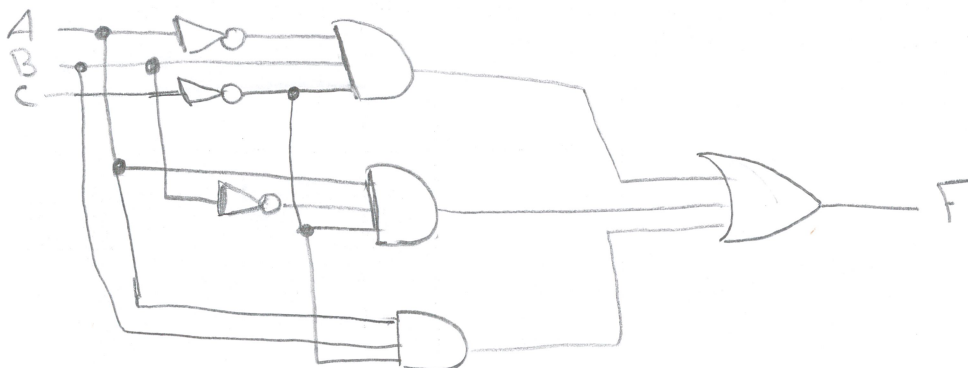TA Initials: MS