

**P1. (10 points)**

Consider a basic SR latch with inputs  $S$ ,  $R$ , and outputs  $Q_a$ ,  $Q_b$ . (Figure 5.4 in textbook)

- (5 points) What would happen to  $Q_a$  and  $Q_b$  if  $S=R=1$ ?
- (5 points) What would happen to  $Q_a$  and  $Q_b$  if we transit from  $S=R=1$  to  $S=R=0$ ?

Solution:

a)

$S=R=1$  will cause  $Q_a = Q_b = 0$ .


b)

Oscillation will occur. When  $S=R=1$ , we have  $Q_a = Q_b = 0$ . If the next transition is  $S=R=0$ , we have  $Q_a = Q_b = 1$ , which immediately sets  $Q_a = Q_b = 0$ , and so on.

**P2. (15 points)**

Complete the following timing diagram for  $Q_a$ ,  $Q_b$ , and  $Q_c$ , which are the outputs of a gated D latch, a positive edge-triggered D flip-flop, and a negative edge-triggered D flip-flop. Assume  $Q = 0$  initially and no gate delays. (5 points each)


Solution:

 

**P3. (10 points)**

Complete the following timing diagram for a T flip-flop. Assume no gate delays.

Solution:

 

**P4. (10 points)**

The following truth table can be used to construct a T flip-flop using a D flip-flop.


T	Output		D
	Q(t)	Q(t+1)	
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

- (5 points) Write down the simplified SOP expression of D using T and Q(t) for inputs.
- (5 points) Draw the circuit for a T flip-flop using a D flip-flop and other necessary gates.  
Make sure you connect the flip-flop to a clock signal.

Solution:

a)  $D = T'Q(t) + TQ'(t)$

b)

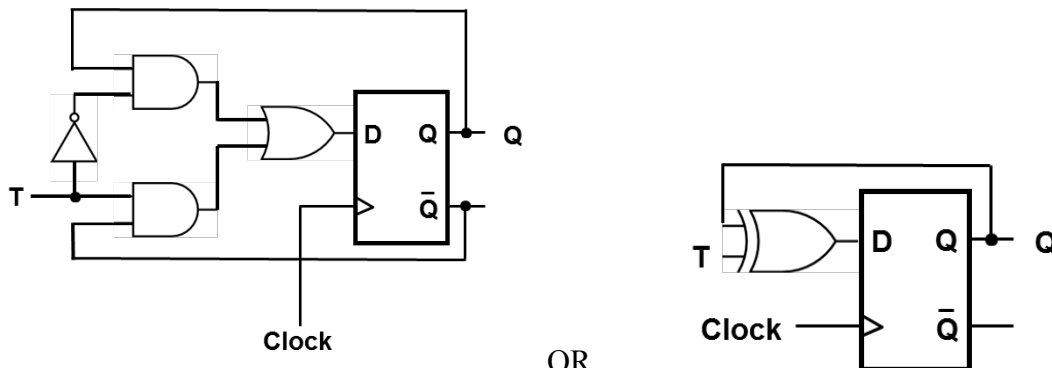

**P5. (20 points)**

Construct a JK flip-flop using a T flip-flop.

- (10 points) Complete the following truth table.
- (5 points) Write down the simplified SOP expression of T using J, K, and  $Q(t)$  for inputs.
- (5 points) Draw the circuit for a JK flip-flop using a T flip-flop and other necessary gates.  
Make sure you connect the flip-flop to a clock signal.


Solution:

a)

J	K	Output		T
		$Q(t)$	$Q(t+1)$	
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

b)  $T = JQ'(t) + KQ(t)$

c)

 


**P6. (20 points)**


Design a 4-bit shift register that has a control input  $S$ , a data input  $X$ , and output  $Q_3Q_2Q_1Q_0$ .

When  $S=0$ , the register will shift left, i.e., the output becomes  $Q_2Q_1Q_0X$ . When  $S=1$ , the register will shift right and the output becomes  $XQ_3Q_2Q_1$ . Draw a circuit for such a shift register using 4 D flip-flops and 4 2-to-1 multiplexers.

Solution:

 

**P7. (15points)**

 

- (10 points) Complete the truth table for the circuit above.
- (5 points) Based on the truth table, could you identify which flip-flop it is?

Solution:

a)

Input	$Q(t)$	J	K	$Q(t+1)$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	1	0

b) T flip-flop.