

CprE 281: Digital Logic
Midterm 2: Friday Oct 28, 2016

Student Name:

Student ID Number:


Lab Section:	Mon 9-12(N)	Mon 12-3(P)	Mon 5-8(R)	Tue 11-2(U)
(circle one)	Tue 2-5(M)	Wed 8-11(J)	Wed 6-9(T)	Thur 11-2(Q)
	Thur 11-2(V)	Thur 2-5(L)	Thur 5-8(K)	Fri 11-2(G)

1. True/False Questions (10 x 1p each = 10p)

- (a) I forgot to write down my name and student ID number. TRUE / FALSE
- (b) When $T=1$ the output of a T flip-flop divides the frequency of the clock by 2. TRUE / FALSE
- (c) Any Boolean function can be implemented using only 2-to-4 decoders. TRUE / FALSE
- (d) The outputs of a code converter are one-hot encoded. TRUE / FALSE
- (e) The select lines of an 8-to-1 multiplexer are one-hot encoded. TRUE / FALSE
- (f) A D flip-flop can be implemented with only 6 NOR gates. TRUE / FALSE
- (g) In 2's complement notation: $0101 + 1101 = 0010$. TRUE / FALSE
- (h) In sign and magnitude notation: $0000 < 1000$. TRUE / FALSE
- (i) The total delay through a half-adder is 2 gate delays. TRUE / FALSE
- (j) A D flip-flop can be implemented with a T flip-flop and one XOR gate. TRUE / FALSE

 2. Minimization using a K-map (5p)

Draw the K-map for the function $f(a,b,c,d) = \sum m(3,6,7,8,12,15) + D(4,13,14)$.
Then use the K-map to derive the minimized SOP expression for the function f.




$$f = \bar{a}cd + a\bar{c}\bar{d} + cb$$


3. Basic Circuits (3p + 4p + 4p + 4p = 15p).

In all sub-problems, draw the complete wiring diagram using logic gates (no high-level graphical symbols allowed in this problem). Clearly label all inputs and outputs.


(a) 1-to-2 decoder with enable.

 


(b) 2-to-1 multiplexer.

 

(c) Full-adder

 

 (d) Gated D Latch (with NOR gates for the latch).



4. Number Conversions (3p + 4p + 4p + 4p = 15p)

(a) Convert 175_{10} to binary:

$$10101111_2 = 175_{10}$$

$$\begin{array}{rcl} 175/2 & = & 87 \quad 1 \\ 87/2 & = & 43 \quad 1 \\ 43/2 & = & 21 \quad 1 \\ 21/2 & = & 10 \quad 1 \\ 10/2 & = & 5 \quad 0 \\ 5/2 & = & 2 \quad 1 \\ 2/2 & = & 1 \quad 0 \\ 1/2 & = & 0 \quad 1 \end{array}$$

(b) Convert the following 32-bit float number (in IEEE 754 format) to decimal

$$\begin{array}{c} \text{negative} \quad \underbrace{1100000000}_{128} \quad \underbrace{1}_{0.5} \quad \underbrace{100000000000000000000000000000}_{0.25} \end{array}$$

$$(-1)^1 \times 2^{128-127} \times (1 + 0.5 + 0.25) = (-1) \times 2^1 \times 1.75 = -3.5$$

(c) Write down the 32-bit floating point representation (in IEEE 754 format) for 14.0

$$\begin{array}{r} 14/8 = 1.75 \\ -8 \\ \hline 60 \\ -56 \\ \hline 40 \\ -40 \\ \hline 0 \end{array}$$

$$(-1)^0 \times 2^3 \times 1.75 = (-1)^0 \times 2^{130-127} \times (1 + 0.5 + 0.25)$$

$$0 \mid 10000010 \mid 1100 \dots 00$$

21 zeros

(d) Write down the 32-bit floating point representation (in IEEE 754 format) for -0.75

$$-1.5 \times \frac{1}{2} = -0.75 \Rightarrow (-1)^1 \times 2^{-1} \times (1 + 0.5)$$


$$1 \mid 01111110 \mid 100 \dots 00$$

22 zeros

5. Implementation Using an Adder (5p + 5p = 10p)

a) Let $A=(a_3, a_2, a_1, a_0)$ and $B=(b_3, b_2, b_1, b_0)$ be two 4-bit numbers. Draw a circuit that uses the 5-bit adder shown below and any other basic logic gates (ANDs, ORs, or NOTs) to compute the value of D , where $D = A - B$. Clearly label all inputs and outputs.

(5p)

 

b) Explain your solution.


(5p)

The subtraction is implemented as addition in 2's complement. Thus, we need to compute the 2's complement of B . This can be done by computing its 1's complement by inverting all bits and then adding 1. The inversion is performed by the NOT gates. The 1 is added as the c_0 carry bit of the adder. Because this is a 5-bit adder both A and B are padded with one zero on the left (most significant bit)


6. Flip-Flops and Timing Diagrams (3 x 5p = 15p)

Complete the timing diagram for the specified flip-flop such that the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time t_{su} and the hold time t_h are each equal to the width of one square.

 
a) Complete the timing diagram for the D input to a positive-edge triggered D flip-flop.



 b) Complete the timing diagram for the T input to a positive-edge triggered T flip-flop.



 c) Complete the timing diagram for the J input to a positive-edge triggered JK flip-flop.




7. Multiplexers (2p + 8p = 10p)

a) Draw the truth table for the function $f = \bar{a}c + bc + ab$

(2p)

a	b	c	$\bar{a}c + bc + ab$	f
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

 b) Implement this function using only 2-to-1 multiplexers and no other logic gates. Assume that the signals a, b, and c are available only in their non-inverted form. (8p)



8. More Multiplexers (2p + 8p = 10p)


a) Draw the truth table for the function $f = ABC + ABD + ACD + BCD$. (2p)

b) Implement the function f using only 4-to-1 multiplexers and no other logic gates.

You can assume that the variables are available in both inverted and non-inverted form.

Clearly label all inputs, pins, and outputs of your circuit. (8p)


A	B	C	D	$ABC + ABD + ACD + BCD$				f
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0
0	1	1	1	0	0	0	1	1
1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	0	1	1	0	0	1	0	1
1	1	0	0	0	0	0	0	0
1	1	0	1	0	1	0	0	1
1	1	1	0	1	0	0	0	1
1	1	1	1	1	1	1	1	1

 


9. Alternative Implementation (10p)

Implement the logic gates AND, NOR, and NOT in three different ways: 1) using a 2-to-1 multiplexer; 2) using a 4-to-1 multiplexer; and 3) using a 2-to-4 decoder. In this problem you are not allowed to use any other logic gates. You can assume that both x and y available in their inverted and non-inverted form, along with the constants 0 and 1. If some implementation is not possible, then indicate that with words. Label all inputs and outputs.

 
a) Implement in three different ways: $f = \text{AND}(x, y)$.



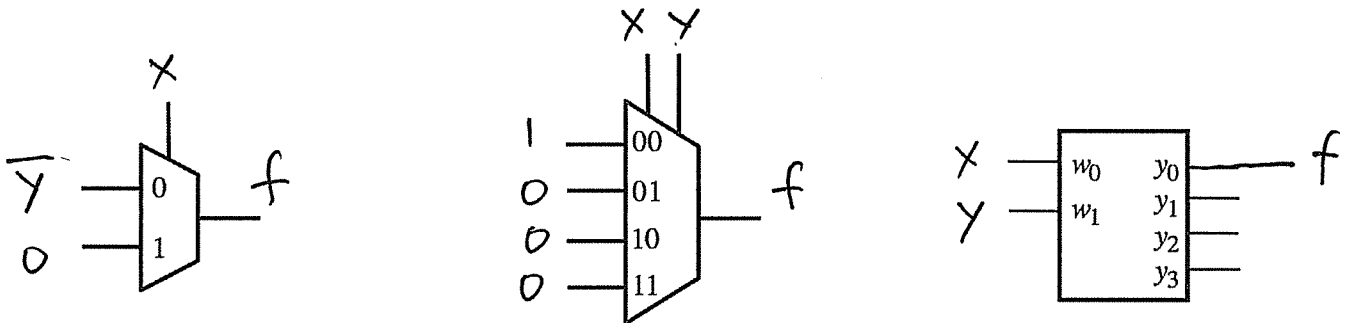b) Implement in three different ways: $f = \text{NOR}(x, y)$.



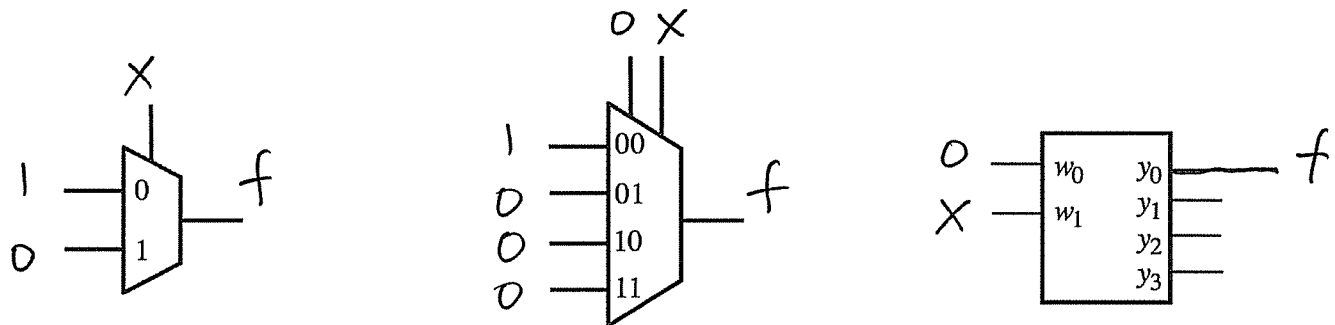
c) Implement in three different ways: $f = \text{NOT}(x)$.



10. Decoder with Multiplexers (5p + 10p = 15p)


- (a) Draw the full (i.e., non-abbreviated) truth table for a 2-to-4 decoder with enable.
 (b) Implement a 2-to-4 decoder with enable using only 2-to-1 multiplexers and no other logic gates. You can assume that the input variables are available in their regular and inverted form, as well as the constants 0 and 1. Label all inputs, output, and pins of your circuit.

E_n	W_1	W_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

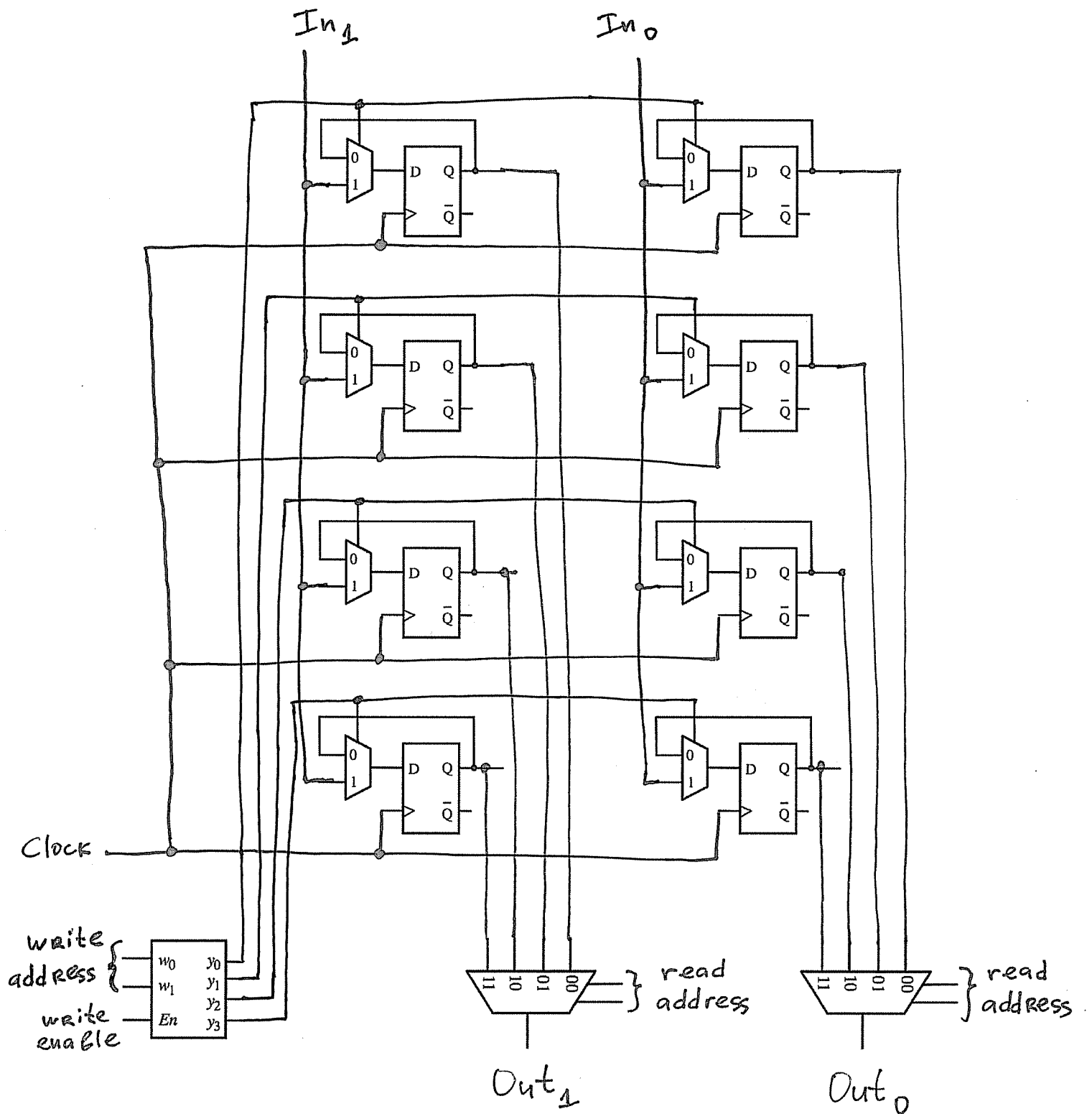11. Register File (15p)

Complete the following circuit diagram to implement a register file with four 2-bit registers, one write port, one read port, and one write enable line. Label all inputs and outputs.



Question	Max	Score
1. True/False	10	
2. K-Map Minimization	5	
3. Basic Circuits	15	
4. Number Conversions	15	
5. Adder Implementation	10	
6. Flip-Flops	15	
7. Multiplexers	10	
8. More Multiplexers	10	
9. Alternative Implementation	10	
10. Decoder with Multiplexers	15	
11. Register File	15	
TOTAL:	130	