


Lab 2 Answer Sheet

Q2. Read section 4.0 and fill in the truth table below for *lab2step2*. Then use it to construct the SOP expression and draw the resulting circuit using logic gates.

Cabbage	Goat	Wolf	Alarm
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

SOP Logic Expression: $A = (\bar{C}\bar{G}\bar{W}) + (\bar{C}\bar{G}W) + (\bar{C}GW) + (C\bar{G}\bar{W}) + (CG\bar{W}) + (CGW)$

Circuit Diagram:

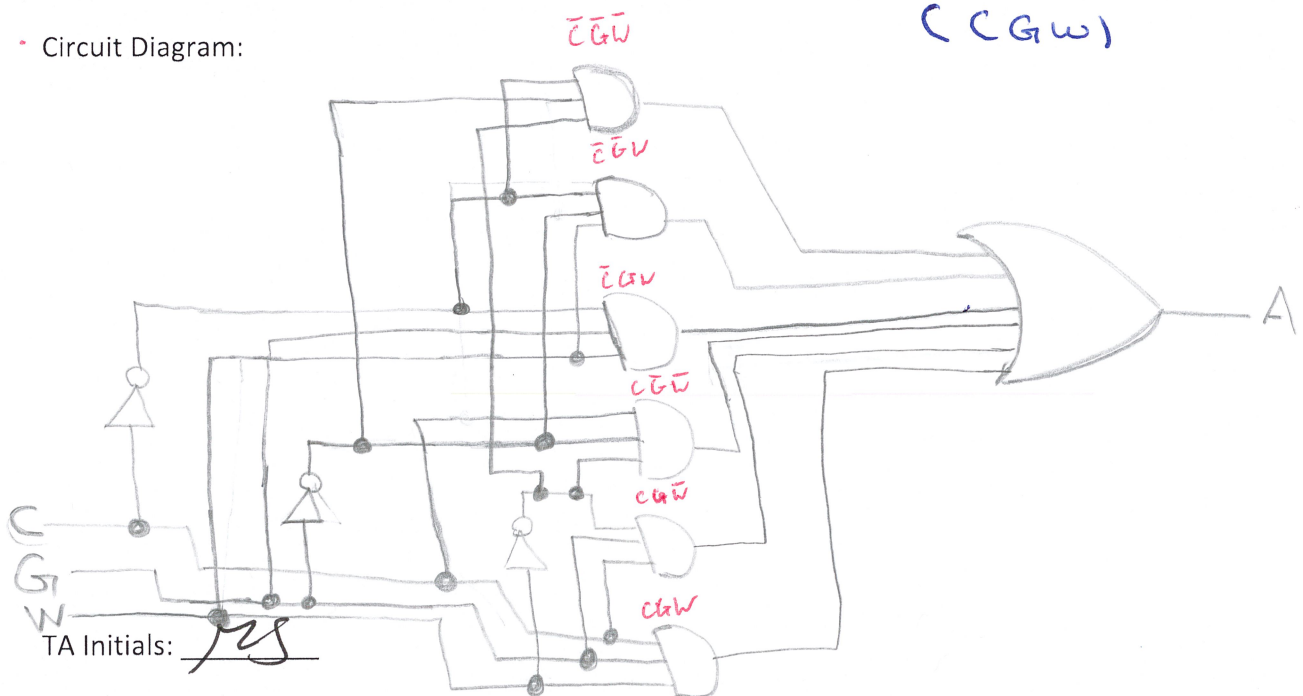

LAB:

3.0 Hardware results demonstrate a correct circuit. TA Initials: AW

4.0 Hardware results demonstrate a correct circuit. TA Initials: AW