

P1. (10 points)

Consider the following logic function:

$$f(A, B, C) = A'BC' + A'BC + AB'C + ABC$$


- (5 points) Show the Shannon's expansion of function F using variable A .
- (5 points) Implement the circuit for function F using one 2-to-1 multiplexer and a minimal number of other logic gates.

Solution:

a)

$$\begin{aligned} f(A, B, C) &= A' \cdot f(0, B, C) + A \cdot f(1, B, C) && \text{Shannon's expansion using } A \\ &= A'(BC' + BC) + A(B'C + BC) \\ &= A'B + AC \end{aligned}$$

b)

 

P2. (20 points)

Consider the following truth table for the function $f(a, b, c, d)$.

a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1

Cpr E 281 HW07 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Combinational-Circuit Building Blocks

Assigned Date: Eighth Week


Due Date: Monday, Oct. 17, 2016

1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


- a) (10 points) Implement f using one 4-to-16 decoder and a minimal number of gates.
b) (10 points) Implement f using one 8-to-1 multiplexer and a minimal number of gates.

Solution:

a)

 

b)

 

P3. (10 points)

Show how to construct a 4-to-16 decoder using five 2-to-4 decoders. Assume each 2-to-4 decoder has an ENABLE input (which enables each decoder).

Solution:

The answer is the same as Figure 4.16 in textbook.

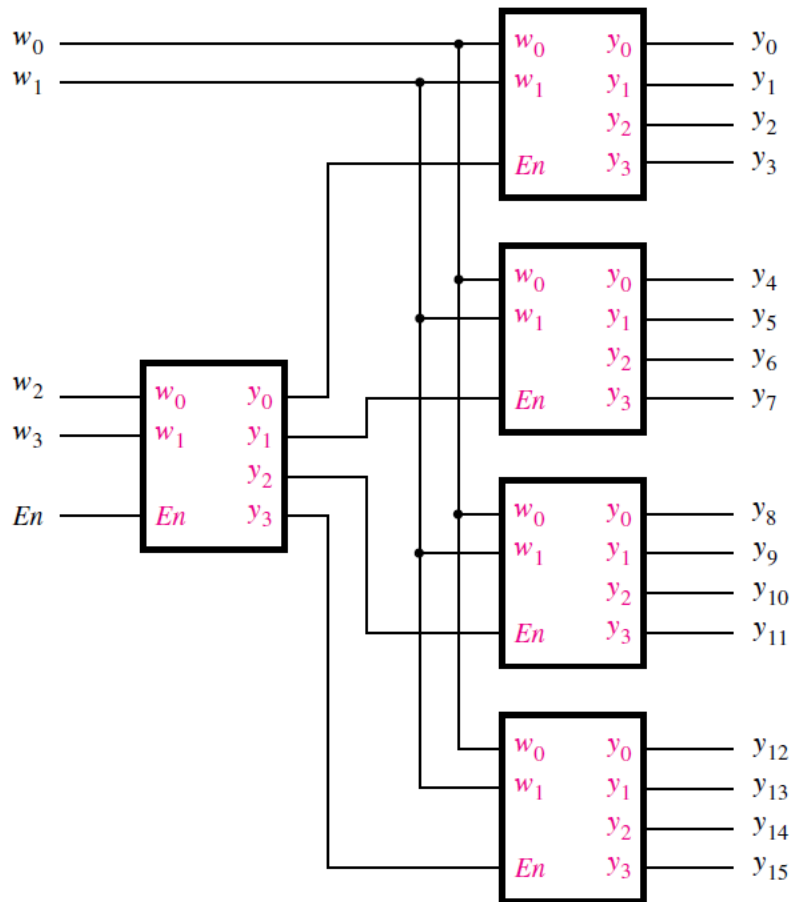


Figure 4.16 A 4-to-16 decoder built using a decoder tree.

Cpr E 281 HW07 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Combinational-Circuit Building Blocks

Assigned Date: Eighth Week


Due Date: Monday, Oct. 17, 2016

P4. (10 points)

Implement the circuit for an 8-to-1 multiplexer using a 3-to-8 decoder and other necessary gates.

The circuit should have control inputs $s_2s_1s_0$, data inputs $w_7w_6w_5w_4w_3w_2w_1w_0$, and an output f .

Solution:

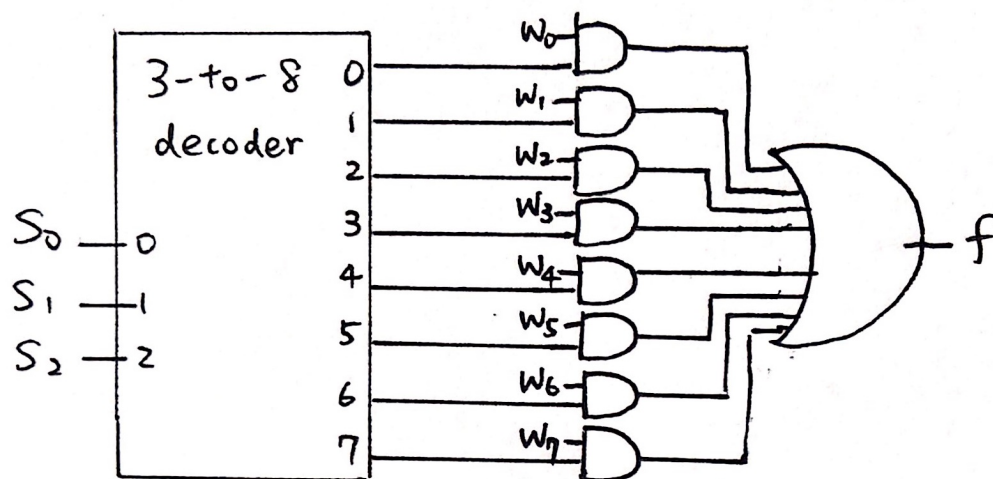

P5. (20 points)

Design a 4-to-2 priority encoder with the same inputs and outputs as in Figure 4.20 in the textbook, but with the following priority order: $w_3 < w_2 < w_1 < w_0$

- (10 points) Show the truth table of this encoder.
- (10 points) Derive the minimal POS expression for y_1 , y_0 , and z , respectively.

Solution:

a)

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
x	x	x	1	0	0	1
x	x	1	0	0	1	1
x	1	0	0	1	0	1
1	0	0	0	1	1	1

b)

$w_1 w_0$ \ $w_3 w_2$		00	01	11	10
		00	01	11	10
00		d	1	1	1
01		0	0	0	0
11		0	0	0	0
10		0	0	0	0

w_0'

w_1'

$$y_1 = w_1' w_0'$$

$$z = w_3 + w_2 + w_1 + w_0$$

$w_1 w_0$ \ $w_3 w_2$		00	01	11	10
		00	01	11	10
00		d	0	0	1
01		0	0	0	0
11		0	0	0	0
10		1	1	1	1


w_0'

$$y_0 = (w_2' + w_1) w_0'$$

P6. (10 points)

Complete the following timing diagram for a gated SR-latch. Assume there's no gate delay.

Solution:

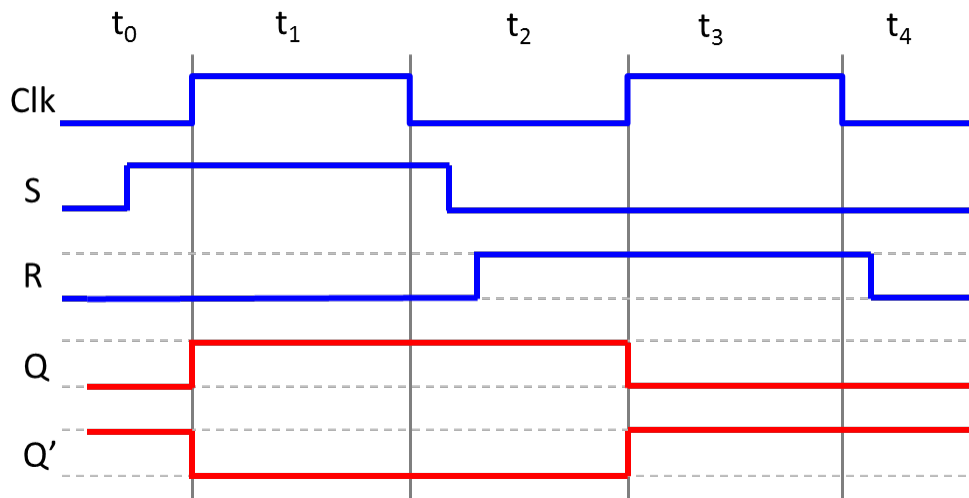

P7. (20 points)

A full-adder (FA) has the following truth table:

x	y	c_{in}	s	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- (10 points) Implement the circuit for output s by using one 4-to-1 multiplexer and a minimal number of gates.
- (10 points) Implement the circuit for output c_{out} by using one 4-to-1 multiplexer. Please use x and y as control inputs s_1 and s_0 for the multiplexer.

Cpr E 281 HW07 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY


Combinational-Circuit Building Blocks

Assigned Date: Eighth Week

Due Date: Monday, Oct. 17, 2016

Solution:

a)

 

b)

