

P1. (10 points)

Design the modulo-5 counter which counts in the sequence 0, 1, 2, 3, 4, 0, 1, 2, 3, 4... when input $w=1$, and stops counting when $w=0$. Use D flip-flops in your circuit.

Solution:

Grading criteria

(3 points) state-assigned table

(3 points) simplified logic expressions for next state and output

(4 points) circuit diagram


State table

Present State	Next State		Output
	$w=0$	$w=1$	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	A	4

State-assigned table

Present State	Next State		Output
	$w=0$	$w=1$	
$y_2 y_1 y_0$	$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	$z_2 z_1 z_0$
A 0 0 0	0 0 0	0 0 1	0 0 0
B 0 0 1	0 0 1	0 1 0	0 0 1
C 0 1 0	0 1 0	0 1 1	0 1 0
D 0 1 1	0 1 1	1 0 0	0 1 1
E 1 0 0	1 0 0	0 0 0	1 0 0
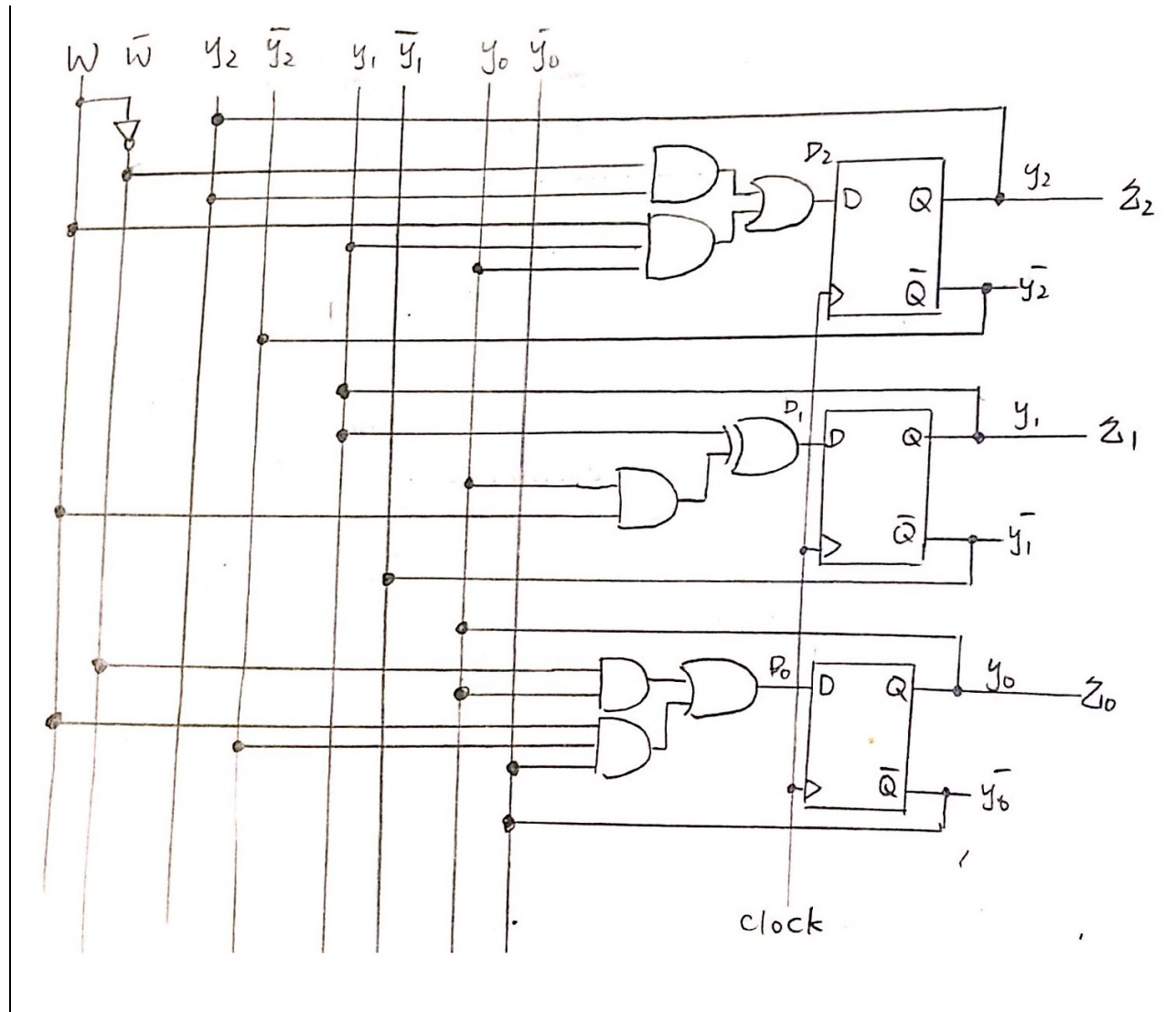
$$\begin{cases} D_2 = Y_2 = \bar{w}y_2 + wy_1y_0 \\ D_1 = Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_1\bar{y}_0 = wy_0 \oplus y_1 \\ D_0 = Y_0 = \bar{w}y_0 + wy_2\bar{y}_0 \\ z_2 = y_2, z_1 = y_1, z_0 = y_0 \end{cases}$$




P2. (10 points)

Repeat P1 using T flip-flops.

Solution:


Present State $y_2 y_1 y_0$	Next State		T Flip-Flops		
	$W=0$ $y_2 y_1 y_0$	$W=1$ $y_2 y_1 y_0$	$W=0$ $T_2 T_1 T_0$	$W=1$ $T_2 T_1 T_0$	
0 0 0	0 0 0	0 0 1	0 0 0	0 0 1	$T_2 = W y_2 + W y_1 y_0$ $T_1 = W y_0$ $T_0 = W \bar{y}_2$
0 0 1	0 0 1	0 1 0	0 0 0	0 1 1	
0 1 0	0 1 0	0 1 1	0 0 0	0 0 1	
0 1 1	0 1 1	1 0 0	0 0 0	1 1 1	
1 0 0	1 0 0	0 0 0	0 0 0	1 0 0	

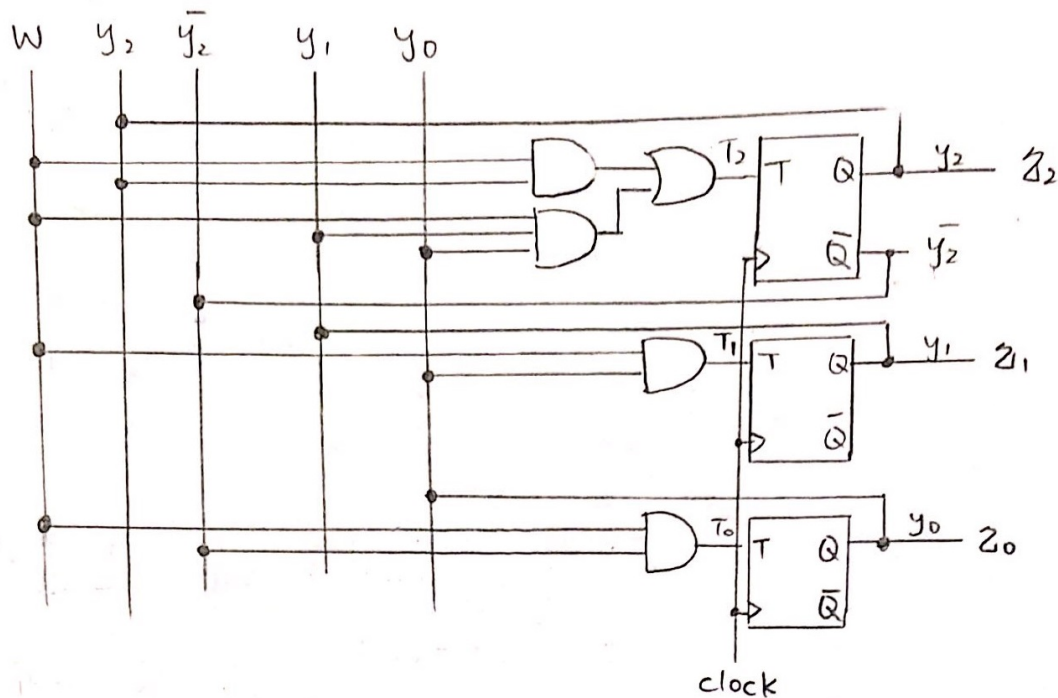

P3. (10 points)

Repeat P1 using JK flip-flops.

Solution:

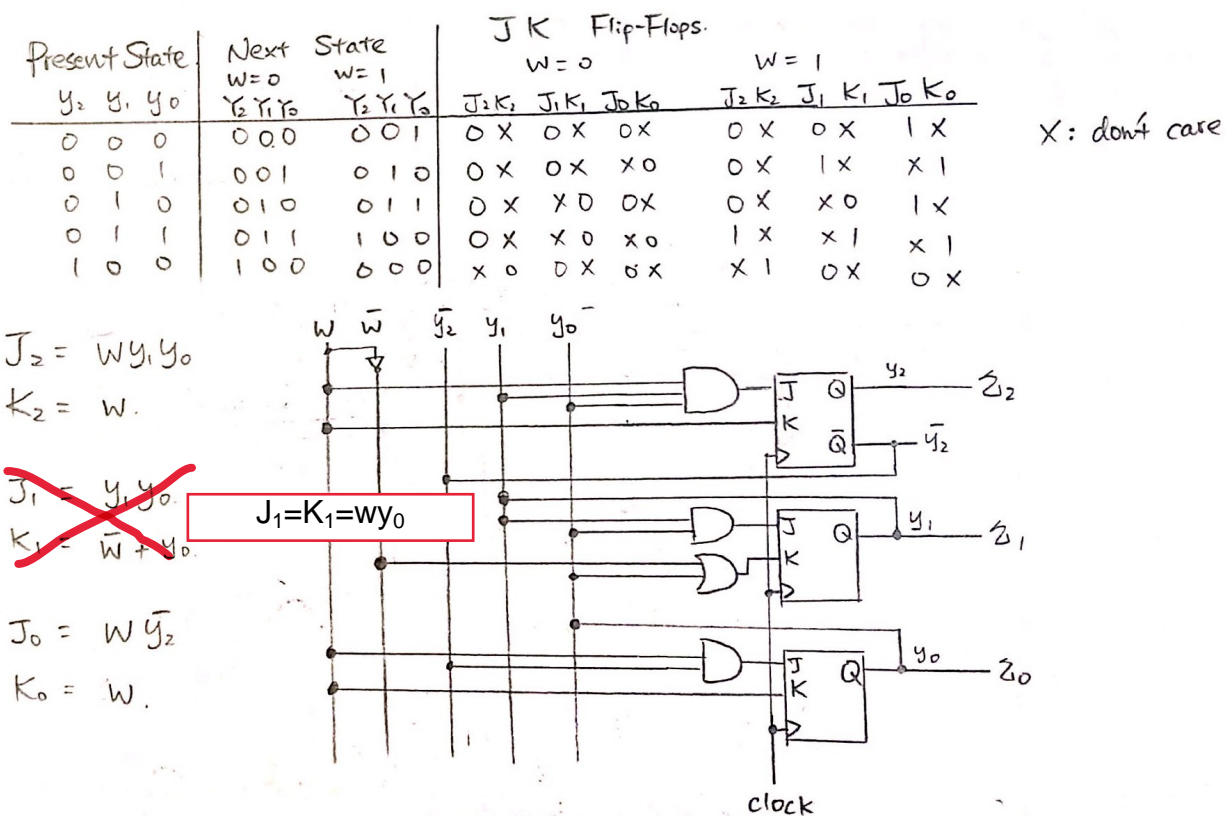

P4. (10 points)

Design the modulo-12 up-counter which counts in the sequence 0, 1, 2, 3, ..., 9, 10, 11, 0.... with input w as an enable. Use JK flip-flops in your circuit.

Solution:

	Present State $y_3 y_2 y_1 y_0$	Next State		JK Flip-Flops							
		$w=0$ $Y_3 Y_2 Y_1 Y_0$	$w=1$ $Y_3 Y_2 Y_1 Y_0$	$w=0$				$w=1$			
				$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
0	0 0 0 0	0 0 0 0	0 0 0 1	0 x	0 x	0 x	0 x	0 x	0 x	0 x	1 x
1	0 0 0 1	0 0 0 1	0 0 1 0	0 x	0 x	0 x	x 0	0 x	0 x	1 x	x 1
2	0 0 1 0	0 0 1 0	0 0 1 1	0 x	0 x	x 0	0 x	0 x	0 x	x 0	1 x
3	0 0 1 1	0 0 1 1	0 1 0 0	0 x	0 x	x 0	x 0	0 x	1 x	x 1	x 1
4	0 1 0 0	0 1 0 0	0 1 0 1	0 x	x 0	0 x	0 x	0 x	x 0	0 x	1 x
5	0 1 0 1	0 1 0 1	0 1 1 0	0 x	x 0	0 x	x 0	0 x	x 0	1 x	x 1
6	0 1 1 0	0 1 1 0	0 1 1 1	0 x	x 0	x 0	0 x	0 x	x 0	x 0	1 x
7	0 1 1 1	0 1 1 1	1 0 0 0	0 x	x 0	x 0	x 0	1 x	x 1	x 1	x 1
8	1 0 0 0	1 0 0 0	1 0 0 1	x 0	0 x	0 x	0 x	x 0	0 x	0 x	1 x
9	1 0 0 1	1 0 0 1	1 0 1 0	x 0	0 x	0 x	x 0	x 0	0 x	1 x	x 1
10	1 0 1 0	1 0 1 0	1 0 1 1	x 0	0 x	x 0	0 x	x 0	0 x	x 0	1 x
11	1 0 1 1	1 0 1 1	0 0 0 0	x 0	0 x	x 0	x 0	x 1	0 x	x 1	x 1
12	1 1 0 0										
13	1 1 0 1										
14	1 1 1 0										
15	1 1 1 1										


Doing 5-variable K maps to get $J_3 K_3$, $J_2 K_2$, $J_1 K_1$, and $J_0 K_0$.

$$\Rightarrow \begin{cases} J_3 = w y_2 y_1 y_0 \\ K_3 = w y_1 y_0 \end{cases} \quad \begin{cases} J_2 = w \bar{y}_3 y_1 y_0 \\ K_2 = w y_1 y_0 \end{cases} \quad J_1 = K_1 = w y_0 \quad J_0 = K_0 = \bar{w}$$

Cpr E 281 HW11 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

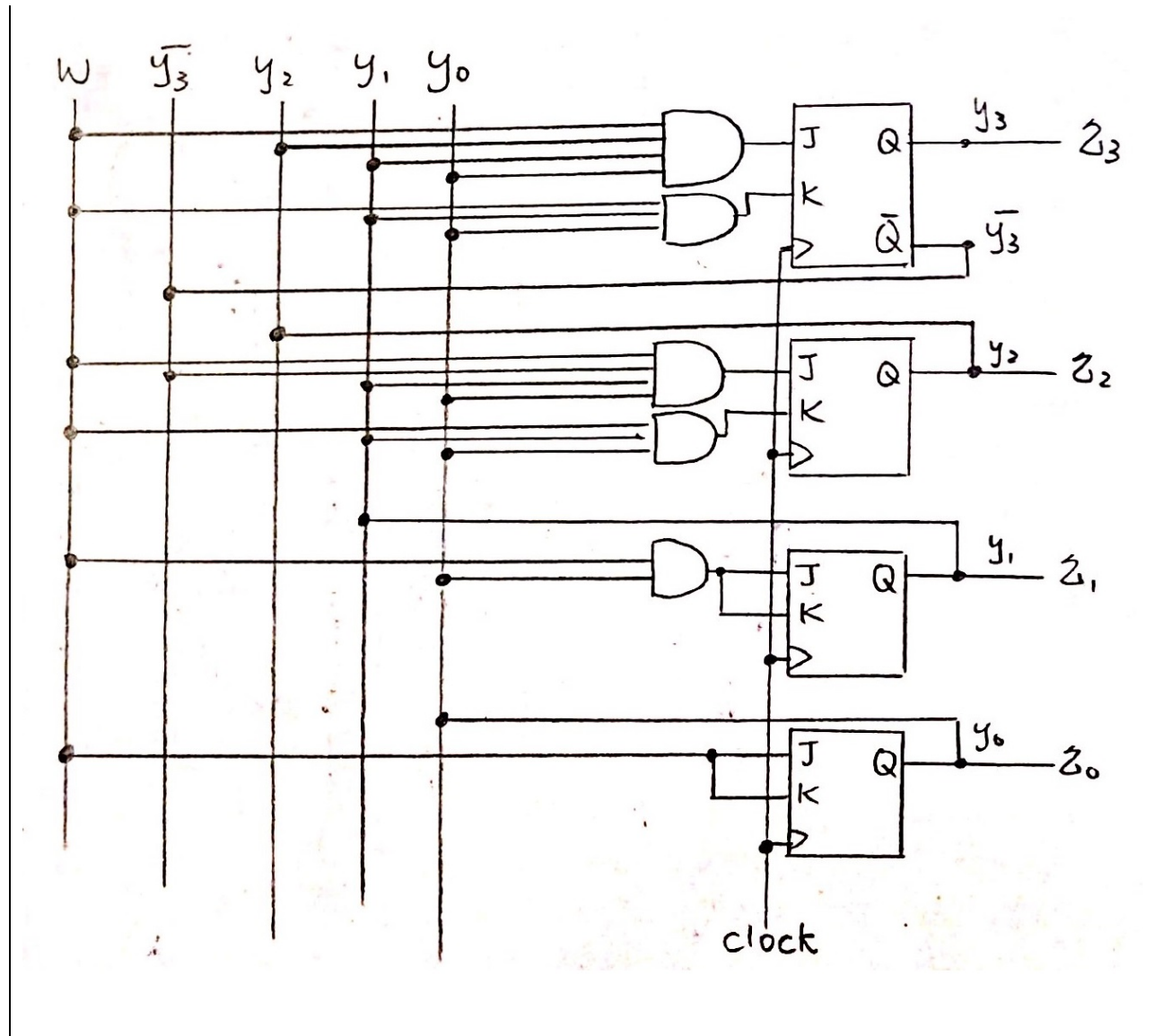Synchronous Sequential Circuits
Assigned Date: Thirteenth Week
Due Date: Monday, Nov. 28, 2016




P5. (40 points)

A counter has a special counting sequence: 0, 5, 7, 1, 0, 5, 7, 1, and so on. Design this counter with minimal number of states.

- (5 points) Draw a state diagram for the counter.
- (5 points) Construct a state-assigned table including the next state and output.
- (10 points) Draw the circuit diagram for the counter using D flip-flops.
- (10 points) Repeat (c) using T flip-flops.
- (10 points) Repeat (c) using JK flip-flops.

Solution:

This counter does not require an enable. Students may have different state assignments from this solution which could also be a correct approach.

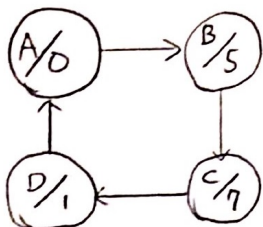
a)  (optional)

Present State	Next State	Output
A	B	0
B	C	5
C	D	7
D	A	1

b)

Present State $y_1 y_0$	Next State $Y_1 Y_0$	Output $z_2 z_1 z_0$
0 0	0 1	0 0 0
0 1	1 0	1 0 1
1 0	1 1	1 1 1
1 1	0 0	0 0 1

$Y_1 = y_1 \oplus y_0$
 $Y_0 = \bar{y}_0$
 $z_2 = y_1 \oplus y_0 = Y_1$
 $z_1 = y_1 \bar{y}_0$
 $z_0 = y_1 + y_0$

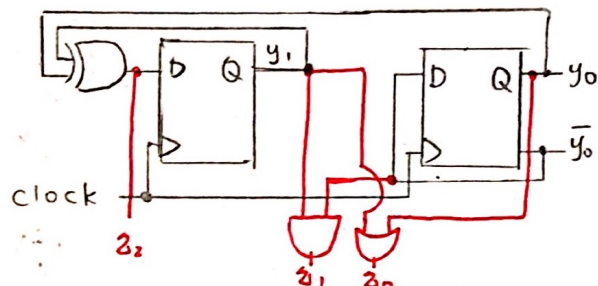c) 

Cpr E 281 HW11 SOLUTION


ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Synchronous Sequential Circuits
Assigned Date: Thirteenth Week
Due Date: Monday, Nov. 28, 2016

d)

Present State $y_1 y_0$	Next State $Y_1 Y_0$	T Flip-Flops $T_1 T_0$
0 0	0 1	0 1
0 1	1 0	1 1
1 0	1 1	0 1
1 1	0 0	1 1

 
$$\Rightarrow \begin{cases} T_1 = y_0 \\ T_0 = 1 \end{cases}$$



e)

Present State $y_1 y_0$	Next State $Y_1 Y_0$	J K Flip-Flops $J_1 K_1 J_0 K_0$
0 0	0 1	0 x 1 x
0 1	1 0	1 x x 1
1 0	1 1	x 0 1 x
1 1	0 0	x 1 x 1
 
$$\Rightarrow \begin{cases} J_1 = y_0 \\ K_1 = y_0 \end{cases} \quad \begin{cases} J_0 = 1 \\ K_0 = 1 \end{cases}$$




P6. (10 points)

Draw a state transition diagram for:

- (5 points) A state machine that reads in a sequence of binary digits, one at a time, and stops when it has read in a total of five 1s (need not to be consecutive). To “stop” the machine, merely have it loop repeatedly in a final state.
- (5 points) A state machine that stops when it has read in at least three consecutive 1s followed by a 0.

Solution:

 

P7. (10 points) Arbiter Circuits

The arbiter FSM defined in Section 6.8 (Figure 6.72) may cause device 3 to never get serviced if devices 1 and 2 continuously keep raising requests, so that in the Idle state it always happens that either device 1 or device 2 has an outstanding request. Modify the proposed FSM to ensure that device 3 will get serviced, such that if it raises a request, the device 1 and 2 will be serviced only once before the device 3 is granted its request.

Solution:

