

Cpr E 281 LAB3 ELECTRICAL AND COMPUTER ENGINEERING IOWA STATE UNIVERSITY

Lab 3 Answer Sheet

Name and Student ID: Hosam Abdelbauab , 838973172 Lab Section: K

Date: Sept 11, 2016

PRELAB:

*Q1. Read section 3.0 and fill in the truth table below for Design 1 (the farmer's problem). Then use it to construct the POS expression.

	Cabbage	Goat	Wolf	Alarm
-	0	0	0	1
	0	0	1	1
	0	1	0	0
	0	1	1	1
	1	0	0	1
	1	0	1	0
	1	1	0	1
	1	1	1	1

C& G G8W

POS Logic Expression: $A = (C + \overline{G} + W) (\overline{C} + \overline{G} + \overline{w})$

TA Initials: A W

Cpr E 281 LAB3 ELECTRICAL AND COMPUTER ENGINEERING IOWA STATE UNIVERSITY

Lab 3 Answer Sheet

• Q2. Read section 4.0 and fill in the truth table below for Design 2 (adding the farmer). Then use it to construct the SOP expressions.

Farmer	Cabbage	Goat	Wolf	Alarm
0	0	0	0	0
0	0	0	1	0 .
0	0	1	0	
0	0	1	1	112:00
0	1	0	0	
0	1	0	1	0.
0	1	1	0	1 1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	6
1	0	1	1	0
1	1	0	0	11
1	1	0	1	
1	1	1	0	0
1	1	1	1	0

Canonical SOP Logic Expression: $A = (FCGw) + (FCG\overline{w}) + (FCGw$	-
Simplified SOP Logic Expression: $A = FCG + FG + FG + FCG$ (FCG \oplus)	
TA Initials:	

LAB:

3.0 Hardware results demonstrate correct code. TA Initials: Schematic Structural Behavioral

4.0 Hardware results demonstrate correct code. TA Initials: